

Updating NMR Probe Electronics in the Muon g-2 Experiment

Audrey Kvam

University of Washington

September 1, 2014

CONTENTS

- 1 The Muon g-2 Experiment
- 2 The NMR Probe Circuitry
- 3 Upgrading the Circuit
- 4 Building the Circuit
- 5 Future Work

- 1 The Muon g-2 Experiment
- 2 The NMR Probe Circuitry
- 3 Upgrading the Circuit
- 4 Building the Circuit
- 5 Future Work

Background

A particle's magnetic moment $\boldsymbol{\mu}$ is related to its spin \mathbf{S} by

$$\boldsymbol{\mu} = g\mu_B\mathbf{S}, \quad \mu_B = \frac{e\hbar}{2m}$$


For point-like fermions, $g \approx 2$ when radiative corrections are taken into account. The deviation from 2 is called the *anomalous magnetic moment*, and is defined as

$$a = \frac{1}{2}(g - 2).$$


Standard Model Theoretical Prediction

$$a^{\text{SM}} = a^{\text{QED}} + a^{\text{EW}} + a^{\text{Hadron}}$$

- QED

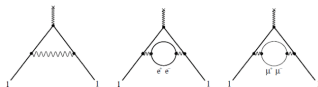

- Hadronic

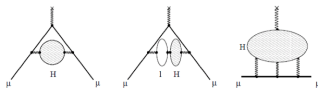

- EW



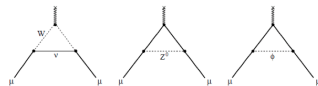


Figure: Radiative corrections to muon g-factor [1].

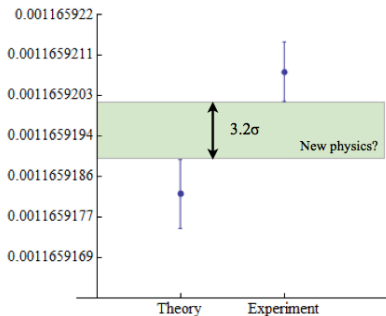

High precision measurements of the magnetic anomaly compared to similarly precise theoretical predictions provide a stringent test of the completeness of the Standard Model.

g-2 at Fermilab


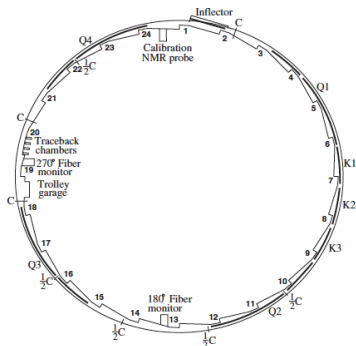


$$\omega_a = \omega_s - \omega_c = -a_\mu \frac{qB}{m}$$

$$a_\mu = \frac{\omega_a / \omega_p}{\mu_\mu / \mu_p - \omega_a / \omega_p}$$


Figure: Storage ring used in g-2 at Brookhaven National Laboratory [3].

Pulsed NMR

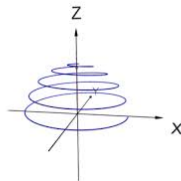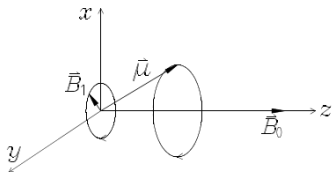

Introduce second, oscillating magnetic field in x-y plane [6].

Relaxation of magnetic field [5].

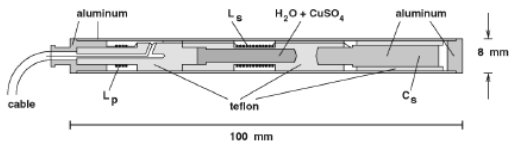

Schematic of NMR probe [1].

The end goal is to measure the returning free induction decay (FID) signal, from which you can extract ω_p .

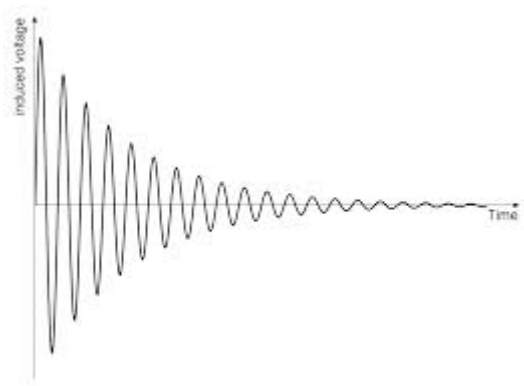


Figure: Shape of ideal FID [4].

Example FID - exponential decay modulated by sine wave. ◀ ☰ ▶ ☰ 🔍 ↻

- 1 The Muon g-2 Experiment
- 2 The NMR Probe Circuitry**
- 3 Upgrading the Circuit
- 4 Building the Circuit
- 5 Future Work

NMR Probe Circuit Diagram





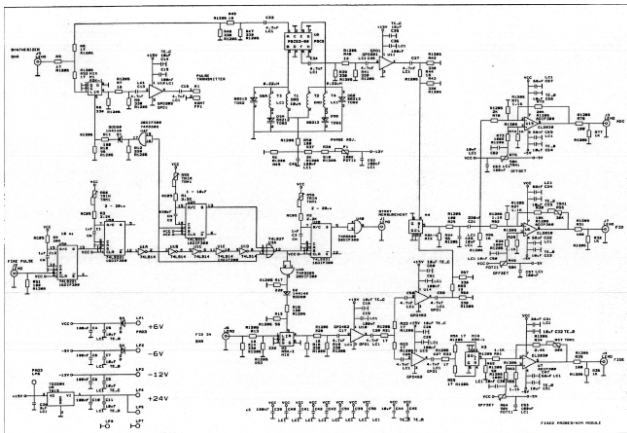



Figure: Schematic of NMR probe circuit [2].

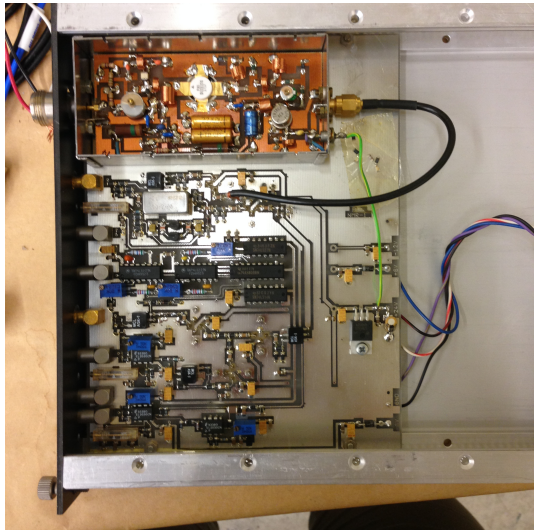

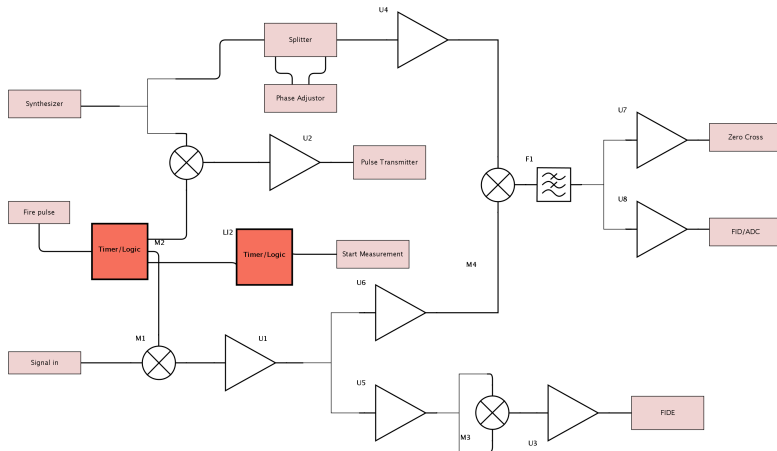

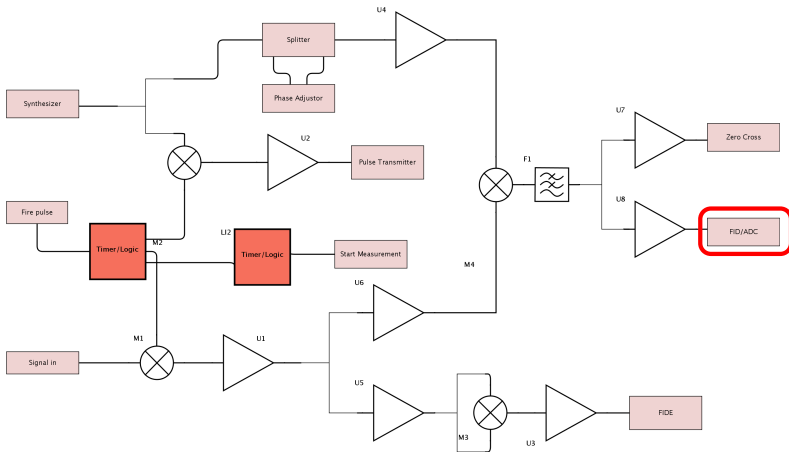


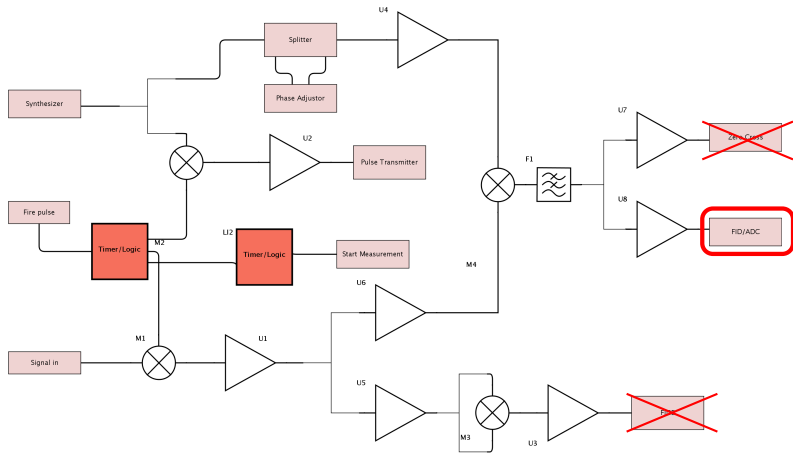

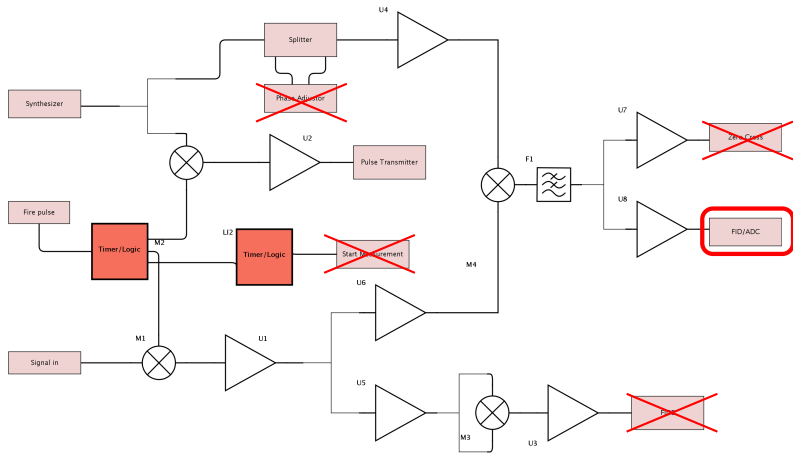


- 1 The Muon g-2 Experiment
- 2 The NMR Probe Circuitry
- 3 Upgrading the Circuit**
- 4 Building the Circuit
- 5 Future Work

New Schematic

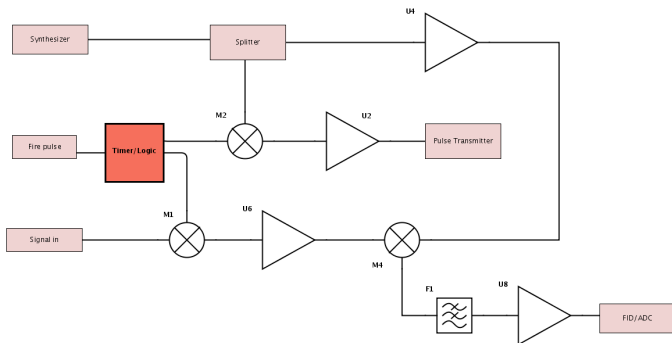


Transmitted Signal

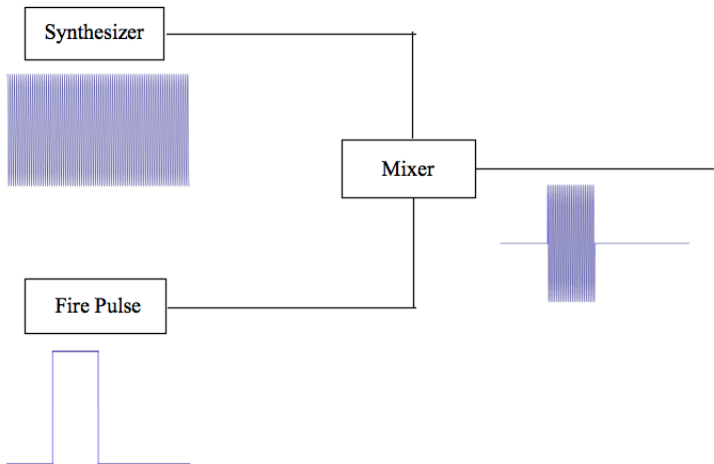

“The LEGOs of RF circuits.” -Erik Swanson

Coaxial
Frequency Mixer
 Level 7 (LO Power +7 dBm) 0.04 to 400 MHz

ZFM-3+




Maximum Ratings

Operating Temperature	-40 to +85°C
Storage Temperature	-55 to +125°C
Power Dissipation	100 mW
DC Voltage	0 to 30V
DC Current	0 to 100 mA

Coaxial Connections

Impedance	50 Ω
Frequency Range	0.04 to 400 MHz

Outline Drawing

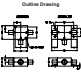

Outline Dimensions (mm)

L	12.7
W	12.7
H	12.7
Pin 1	0.5
Pin 2	0.5
Pin 3	0.5
Pin 4	0.5
Pin 5	0.5
Pin 6	0.5
Pin 7	0.5
Pin 8	0.5
Pin 9	0.5
Pin 10	0.5
Pin 11	0.5
Pin 12	0.5

Features

- Low conversion loss, 2.72 dB typ.
- High LO isolation, 30 dB typ. @ 100 MHz
- Highly matched input

Applications

- RF test
- Receiver & transmitter communications
- Frequency conversion


Electrical Specifications

Frequency (MHz)	Conversion Loss (dB)	LO Isolation (dB)	IP3 (dBm)	1 dB Compression (dBm)
100	2.72	30	10	10
200	2.72	30	10	10
300	2.72	30	10	10
400	2.72	30	10	10

Typical Performance Data

Frequency (MHz)	Conversion Loss (dB)	LO Isolation (dB)	IP3 (dBm)	1 dB Compression (dBm)
100	2.72	30	10	10
200	2.72	30	10	10
300	2.72	30	10	10
400	2.72	30	10	10

Electrical Schematic




Mini-Circuits®




Figure: From [7].

- 1 The Muon g-2 Experiment
- 2 The NMR Probe Circuitry
- 3 Upgrading the Circuit
- 4 Building the Circuit**
- 5 Future Work


Workspace

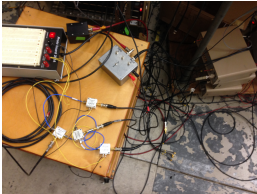

Seeing Signals



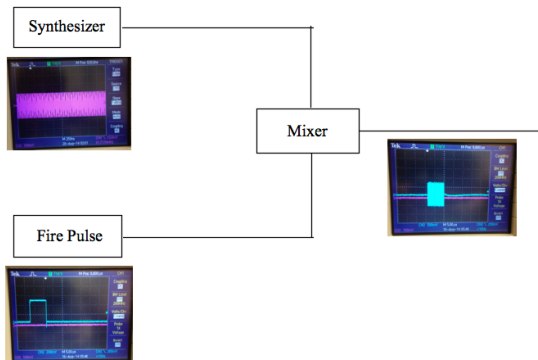


Returning Signal

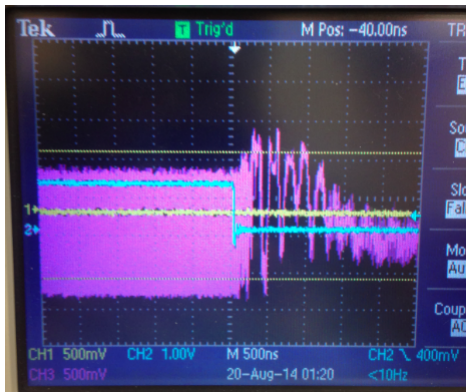


Mix with synthesizer to get FID...

Success

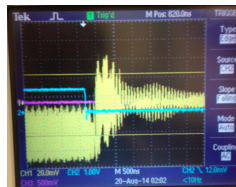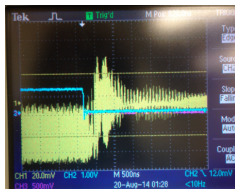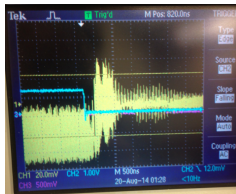

FIDs! With tweaking (adjusting current etc), can look nicer than these.

Final Circuit

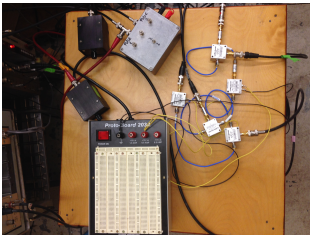

- 1 The Muon g-2 Experiment
- 2 The NMR Probe Circuitry
- 3 Upgrading the Circuit
- 4 Building the Circuit
- 5 Future Work

Making the Circuit Better

- Continue to work with g-2
- Make baseboard for circuit
- Make compatible for experiment
- Additional possibilities
 - Control length of $\frac{\pi}{2}$ pulse
 - Add sequencing of pulses
 - Disentangle relaxation times T_1 and T_2 from spin-echo

Acknowledgments

Thank you very much to Alejandro Garcia and Erik Swanson for their mentorship throughout the summer, and to the entire g-2 group for their help.

Thank you to Alejandro Garcia, Subhadeep Gupta, Linda Vilett, and Janine Nemerever for organizing the INT REU program.

Funding provided by NSF.

References

- [1] Grossmann, Alex P. "Magnetic Field Determination in a Superferricstorage Ring for a Precise Measurement of the Muonmagnetic Anomaly." Thesis. Ruprecht Karl University, 1998. Web.
- [2] R. Prigl et al. PhD thesis, Universitat Heidelberg, 1994.
- [3] G. Bennett et al. [The Muon g-2 Collaboration], *Phys. Rev.* **D 73** (2006) 072003 [arXiv:hep-ex/0602035].
- [4] Wikipedia contributors. "Free induction decay." Wikipedia, The Free Encyclopedia. Wikipedia, The Free Encyclopedia, 2 Jul. 2014. Web. 19 Aug. 2014.
- [5] "NMR-Spektroskopie." Universitt Paderborn:. Department of Chemistry, 15 May 2014. Web. 19 Aug. 2014.
- [6] Stoltenberg, J., D. Pengra, R. Van Dyck, and O. Vilches. "Pulsed Nuclear Magnetic Resonance." (2006) Rutgers University. Web.
- [7] "Coaxial Frequency Mixer." Mini-Circuits: RF/IF and Microwave Components. Mini-Circuits, n.d. Web.